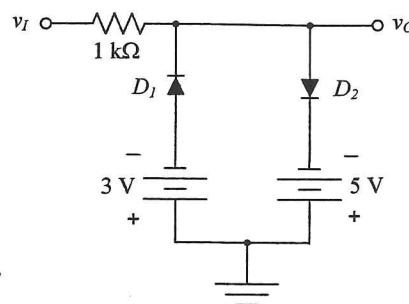


ECE 3200
Test 2
Solutions

- A) The circuit shown below is intended to be a parallel-based clipper, but it has been designed incorrectly. Which of the following changes would correct the design?

- a: Reversing the polarity of the 5 V battery
 b: Reversing the polarity of D_2
 c: Both a and b
 d: Reversing the polarity of the 3 V battery
 e: None of the above



(See text sec. 2.3.1)

The 5V battery should be reversed to create a positive clipping threshold.

- B) Which of the following actions is performed by a clamper circuit?

- a: Eliminating portions of a signal above or below a specified level
 b: Increasing the peak-to-peak amplitude of a signal
 c: Removing low frequency components from a signal
 d: Maintaining the frequency of a periodic signal at a constant value
 e: None of the above

(See text sec. 2.3.2)

A clamper shifts the dc level of a signal without modifying the shape of the waveform.

- C) The parameters of the diodes in the circuit below are $V_f = 0.7$ V and $r_f = 0$. Which of the following is closest to the value of the output voltage v_O when $v_I = 0$ V?


- a: 0 V
 b: 3 V
 c: 6 V
 d: 9 V
 e: 12 V

When $v_I < 5.7$ V,

D_1 is off (open circuit) and D_2 is on.

From KVL, voltage divider,
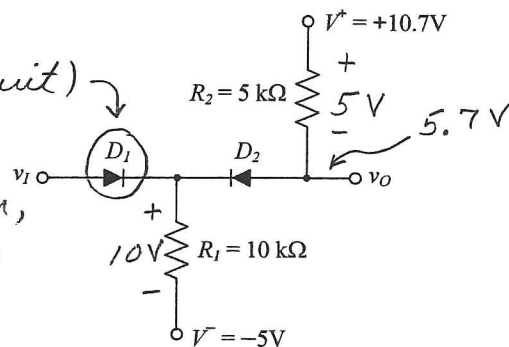
$$v_O = +10.7 \text{ V} - 5 \text{ V} = 5.7 \text{ V}$$



- D) How many pn junctions are contained in a bipolar junction transistor?

- a: 0
 b: 1
 c: 2
 d: 3
 e: None of the above

(See text sec. 5.1)

- 1) BE junction
 2) BC junction

- E) The common-emitter current gain of a bipolar junction transistor is equal to 90. If the transistor is operating in the forward-active mode, and the emitter current is 5.46 mA, which of the following is closest to the value of the collector current?

a: 5.5 mA
 (b): 5.4 mA
 c: 5.3 mA
 d: 5.2 mA
 e: 5.1 mA

$$I_C = \alpha I_E = \left(\frac{\beta}{1+\beta} \right) I_E$$

$$= \left(\frac{90}{1+90} \right) (5.46 \text{ mA}) = 5.4 \text{ mA}$$

- F) The common-emitter current gain of a bipolar junction transistor is equal to 100. If the base current is 100 μA and the emitter current is 1 mA, which of the following is closest to the value of the collector current?

(a): 0.9 mA
 b: 1.0 mA
 c: 1.1 mA
 d: 10.0 mA
 e: 10.1 mA

$$I_E = I_B + I_C \Rightarrow I_C = I_E - I_B$$

$$\Rightarrow I_C = 1 \text{ mA} - 0.1 \text{ mA} = 0.9 \text{ mA}$$

(Note: $I_C \neq \beta I_B \Rightarrow$ Not in F.A. Mode)

- G) In the circuit shown below, $V_{CE} = 4 \text{ V}$. Which of the following is closest to the value of β ?


a: 50
 b: 100
 c: 150
 (d): 200
 e: 250

$$V_{CE} > 0.2 \text{ V} \Rightarrow \text{F.A. Mode}$$

$$I_C = \frac{10 \text{ V} - 4 \text{ V}}{2 \text{ k}\Omega} = 3 \text{ mA}$$

$$I_B = \frac{4 \text{ V} - 0.7 \text{ V}}{220 \text{ k}\Omega} = 0.015 \text{ mA}$$
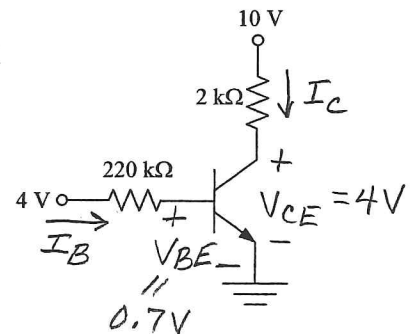
$$\beta = \frac{I_C}{I_B} = \frac{3 \text{ mA}}{0.015 \text{ mA}} = 200$$



- H) For the transistor in the circuit shown below, $\beta = 65$. Current is flowing in the circuit, and $V_{EC} = 1.5 \text{ V}$. Which of the following is closest to the value of the base current?

a: 0.01 mA
 b: 0.02 mA
 (c): 0.03 mA
 d: 0.04 mA
 e: 0.05 mA

Current is flowing and $V_{EC} > 0.2 \text{ V}$


\Rightarrow F.A. Mode

$\Rightarrow V_{EB} = 0.7 \text{ V}$

$$V_C = V_{EB} - V_{EC} = 0.7 \text{ V} - 1.5 \text{ V} = -0.8 \text{ V}$$


$$\Rightarrow I_C = \frac{-0.8 \text{ V} - (-5 \text{ V})}{2 \text{ k}\Omega} = 2.1 \text{ mA}$$
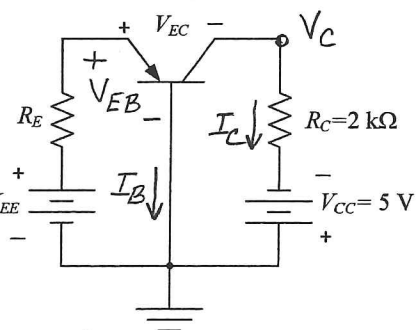
$$\Rightarrow I_B = \frac{I_C}{\beta} = \frac{2.1 \text{ mA}}{65} \approx 0.032 \text{ mA}$$



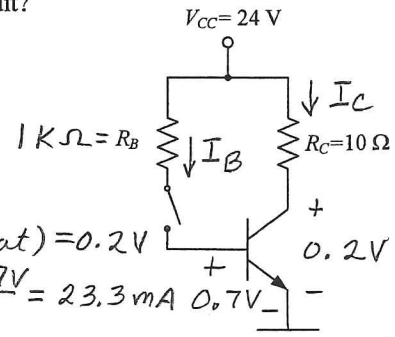- I) The transistor in the circuit below is intended to function as a switch. Three transistors are available: Q_1 , for which $\beta = 90$, Q_2 , for which $\beta = 120$, and Q_3 , for which $\beta = 150$. If $R_B = 1 \text{ k}\Omega$, which of the transistors would be acceptable for use in the circuit?

- a: All three are acceptable.
 b: Q_1 and Q_2 are acceptable, but Q_3 is not.
 c: Q_2 and Q_3 are acceptable, but Q_1 is not.
 d: Q_3 is acceptable, but Q_1 and Q_2 are not.
 e: No transistor is acceptable.



Transistor must be in saturation

when switch is closed $\Rightarrow V_{CE} = V_{CE(sat)} = 0.2 \text{ V}$

$$I_C = \frac{24 \text{ V} - 0.2 \text{ V}}{10 \Omega} = 2.38 \text{ A}, \quad I_B = \frac{24 \text{ V} - 0.7 \text{ V}}{1 \text{ k}\Omega} = 23.3 \text{ mA}$$

$$I_C < \beta I_B \Rightarrow \beta > \frac{I_C}{I_B} = \frac{2.38 \text{ A}}{0.0233 \text{ A}} \approx 102 \quad \text{Note } \beta > 102 \text{ for } Q_2 \text{ \& } Q_3$$

- J) Which of the following values of β will cause the circuit below to be bias stable?


- a: 100
 b: 200
 c: 300
 d: Both a and b
 e: None of the above

Bias stable if

$$R_{TH} < 0.1(1+\beta)R_E$$

$$\Rightarrow \beta > \frac{R_{TH}}{0.1R_E} - 1$$
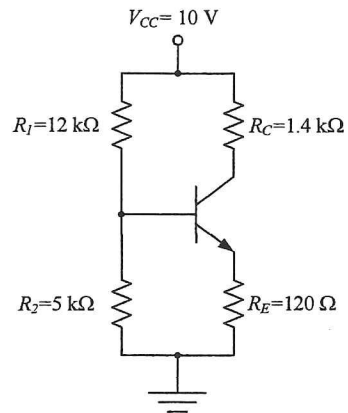
$$\Rightarrow \beta > \frac{(12 \text{ k}\Omega \parallel 5 \text{ k}\Omega)}{(0.1)(0.12 \text{ k}\Omega)} - 1 \approx 293$$



- K) Which of the following are examples of bipolar transistor biasing methods?

- a: Single base resistor biasing and voltage divider biasing
 b: Forward biasing and reverse biasing
 c: Forward-active mode biasing and saturation mode biasing
 d: Thevenin equivalent biasing and Norton equivalent biasing
 e: None of the above

See text sec. 5.4

- L) A pnp BJT with $g_m = 32.2 \text{ mA/V}$ and $r_\pi = 6.2 \text{ k}\Omega$ is biased in the forward-active mode. The transistor's temperature is 300 K. Which of the following is closest to the value of β ?

- a: 120
 b: 140
 c: 160
 d: 180
 e: 200

$$g_m = \frac{I_{CQ}}{V_T} \quad \text{and} \quad r_\pi = \frac{V_T}{I_{BQ}}$$



$$\Rightarrow g_m r_\pi = \left(\frac{I_{CQ}}{V_T} \right) \left(\frac{V_T}{I_{BQ}} \right) = \frac{I_{CQ}}{I_{BQ}} = \beta$$

$$\Rightarrow \beta = (32.2 \frac{\text{mA}}{\text{V}})(6.2 \text{ k}\Omega) \approx 199.6$$

- M) Which of the following amplifiers should have low input resistance and high output resistance?
- a: Voltage amplifiers
 - b: Transconductance amplifiers
 - ☒ c: Current amplifiers
 - d: Transresistance amplifiers
 - e: None of the above
- See text sec. 6.3*

- N) For the transistor in the circuit below, $g_m = 30 \text{ mA/V}$, $V_A = \infty$, and $r_\pi = 1.5 \text{ k}\Omega$. The capacitors have negligible impedance at signal frequencies. Which of the following is closest to the value of R_C that will cause the circuit to have a small-signal, ac voltage gain of -90 ?

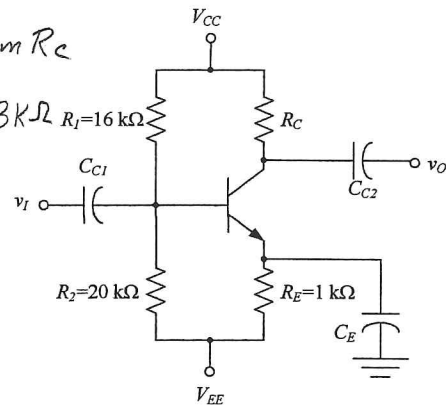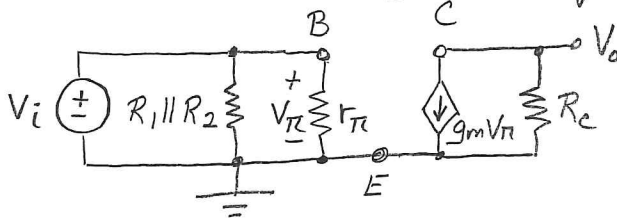- a: 90 k Ω
 - b: 60 k Ω
 - c: 30 k Ω
 - ☒ d: 3 k Ω
 - e: 1 k Ω
- $A_v = \frac{V_o}{V_i} = \frac{-g_m V_\pi R_C}{V_\pi} = -g_m R_C$
- $\Rightarrow R_C = \frac{A_v}{-g_m} = \frac{-90}{-30 \text{ mA/V}} = 3 \text{ k}\Omega$





- O) The transistor in the circuit below is operating in the forward-active mode. Which of the following will happen if the value of R_C is increased?

- a: Both R_i and $|A_v|$ will increase.
- b: R_i will decrease and $|A_v|$ will increase.
- ☒ c: Both R_o and $|A_v|$ will increase.
- d: R_o will increase and $|A_v|$ will remain constant.
- e: None of the above

$R_i = R_1 \parallel R_2 \parallel r_\pi$ (Not dependent on R_C)


$R_o = r_o \parallel R_C$ (Increase)

$|A_v| = | -g_m (r_o \parallel R_C) |$

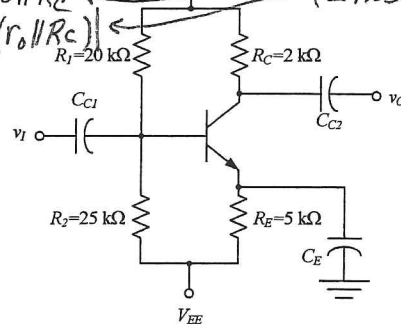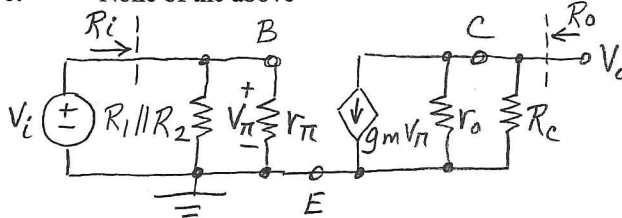


- P) A common-emitter amplifier is constructed using a 12 V dc power supply and a pnp BJT. At the quiescent point, $V_{EC} = 3.89 \text{ V}$ and $I_C = 1.80 \text{ mA}$. If the slope of the circuit's ac load line is $-1 / 1.83 \text{ k}\Omega$, which of the following is closest to the maximum symmetrical swing in the output voltage?

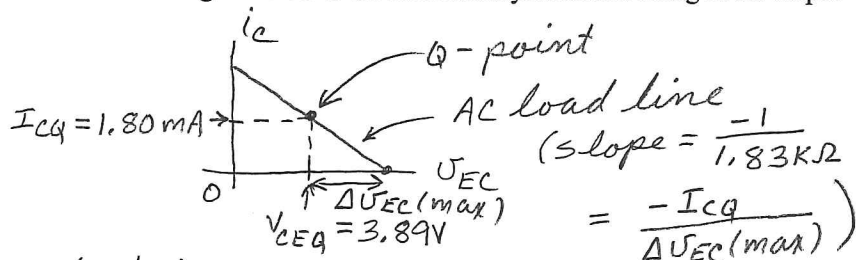- ☒ a: 7 V
- b: 8 V
- c: 9 V
- d: 10 V
- e: 11 V



- Q) For the transistor in the circuit below, $\beta = 100$, $V_A = \infty$, $g_m = 30.5 \text{ mA/V}$, and $r_\pi = 3.28 \text{ k}\Omega$. Which of the following is closest to the small-signal, ac voltage gain of the circuit?

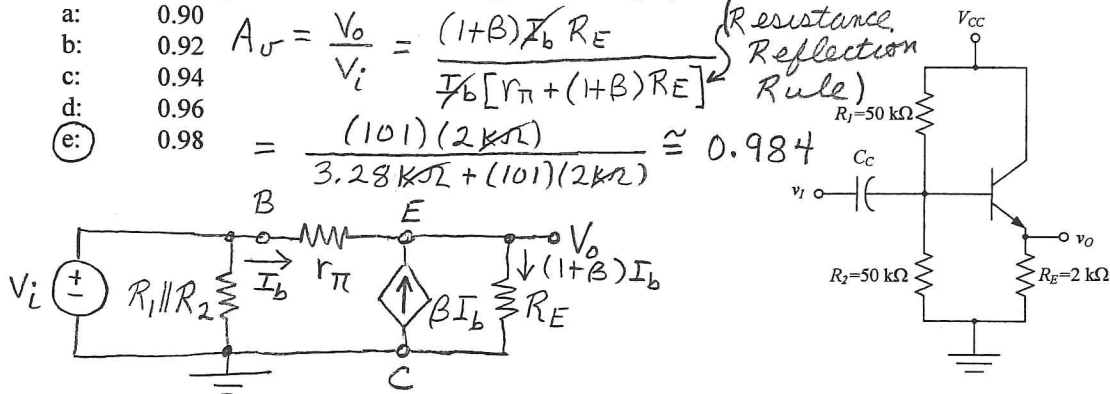
- a: 0.90
b: 0.92
c: 0.94
d: 0.96
e: 0.98



- R) Which of the following are typical properties of the type of circuit below?

- a: Large input resistance and large output resistance
b: Large input resistance and small output resistance
c: Small input resistance and large output resistance
d: Small input resistance and small output resistance
e: None of the above

Common-base amplifier
See text sec. 6.7

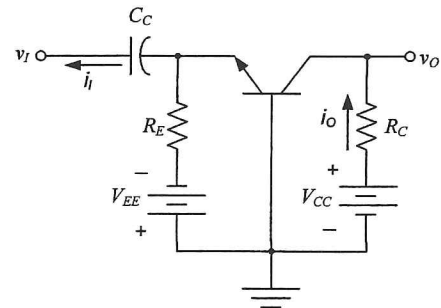

- S) An engineer needs to design a single-transistor amplifier whose small-signal, ac current gain is 20. If the amplifier's input and output resistances are not important for this application, which of the following kinds of amplifiers might be suitable?

- a: Only common-base
b: Either common-emitter or common-collector
c: Either common-base or common-emitter
d: Either common-base or common-collector
e: None of the above

See text sec. 6.8

For common-emitter and common-collector, $A_i > 1$
For common-base, $A_i \approx 1$

- T) For the amplifier below, $V_{CC} = 10 \text{ V}$, $R_C = 3.0 \text{ k}\Omega$, and the quiescent collector current is 2.0 mA . If the power dissipated by the bias resistors is negligible, which of the following is closest to the total average power delivered to the circuit by the power supply?

- a: 0 mW
b: 5 mW
c: 10 mW
d: 15 mW
e: 20 mW

Average power delivered by V_{CC}

$= V_{CC} I_{CQ}$

$= (10 \text{ V})(2.0 \times 10^{-3} \text{ A}) = 0.02 \text{ W}$

