

ECE 3200
Test 1
Solutions

- A) A sample of silicon at $T = 300 \text{ K}$ is doped with phosphorus at a concentration of $1.30 \times 10^{16} \text{ cm}^{-3}$. Which of the following is closest to the minority carrier concentration?

a: 10^{16} cm^{-3}
 b: 10^{10} cm^{-3}
 c: 10^4 cm^{-3}
 d: 10^3 cm^{-3}
 e: 10^2 cm^{-3}

Phosphorus is a donor impurity
 $\Rightarrow n_0 \approx N_d = 1.30 \times 10^{16} \text{ cm}^{-3}$
and holes are minority carriers

$$\Rightarrow p_0 = \frac{n_i^2}{n_0} \approx \frac{(1.5 \times 10^{10} \text{ cm}^{-3})^2}{1.30 \times 10^{16} \text{ cm}^{-3}} \approx 1.7 \times 10^4 \text{ cm}^{-3}$$

- B) Which of the following is true for a sample of semiconductor material if it is doped with a donor impurity?

a: The sample contains more electrons than protons.
 b: The sample is n-type.
 c: The sample has a negative electric charge.
 d: All of the above
 e: None of the above

See text sec. 1.1.2

Doping with donor produces free electrons
 \Rightarrow Free electron concentration is greater than hole concentration \Rightarrow n-type
 (Total # electrons = # protons \Rightarrow No charge)

- C) Which of the following is closest to the concentration of holes in a sample of pure germanium at a temperature of 250 K?

a: 10^{12} cm^{-3}
 b: 10^{11} cm^{-3}
 c: 10^{10} cm^{-3}
 d: 10^9 cm^{-3}
 e: 10^8 cm^{-3}

$n_i = B T^{3/2} e^{\left(\frac{-E_g}{2KT}\right)}$
 $= (1.66 \times 10^{15} \text{ cm}^{-3} \text{ K}^{-3/2}) (250 \text{ K})^{3/2} e^{\left(\frac{-0.66 \text{ eV}}{2(86 \times 10^{-6} \frac{\text{eV}}{\text{K}})(250 \text{ K})}\right)}$
 $\approx 1.42 \times 10^{12} \text{ cm}^{-3}$

- D) Which of the following is closest to the thermal voltage at a temperature of 350 K?

a: 26 mV
 b: 27 mV
 c: 28 mV
 d: 29 mV
 e: 30 mV

$$V_T = \frac{KT}{e} = \frac{(86 \times 10^{-6} \frac{\text{eV}}{\text{K}})(350 \text{ K})}{e}$$

$\approx 0.0301 \text{ V}$

- E) I_F is the current flowing through a certain diode at room temperature when a voltage of 0.2 V is applied across the diode in the forward-bias direction. I_R is the current flowing through the same diode at room temperature when a voltage of 0.2 V is applied across the diode in the reverse-bias direction. Which of the following is closest to the magnitude of the ratio of I_F to I_R ?

- a: 2,400
 (b): 2,200
 c: 2,000
 d: 1,800
 e: 1,600

$$I_D = I_S \left[e^{(V_D/V_T)} - 1 \right]$$

$$\Rightarrow \left| \frac{I_F}{I_R} \right| = \left| \frac{I_S [e^{(0.2V/0.026V)} - 1]}{I_S [e^{(-0.2V/0.026V)} - 1]} \right|$$

$$\cong \left| \frac{2,190}{-1} \right| = 2,190$$


- F) Diodes D_1 and D_2 are forward-biased and connected in parallel in a circuit. The diodes have identical reverse-bias saturation currents, but D_1 has a larger emission coefficient than D_2 . Which of the following statements is true?

- (a): D_1 conducts less current than D_2 .
 b: The voltage across D_1 is smaller than the voltage across D_2 .
 c: Both a and b are true.
 d: D_1 conducts more current than D_2 .
 e: None of the above

Diodes in parallel \Rightarrow Same V_D


$$I_D = I_S \left[e^{\frac{V_D}{nV_T}} - 1 \right]$$

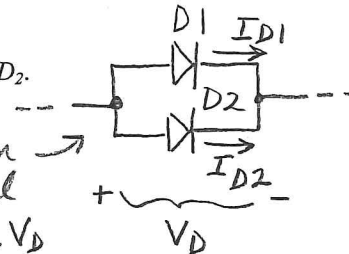Same I_S for both diodes \Rightarrow D_1 has larger value of n \Rightarrow D_1 has smaller I_D



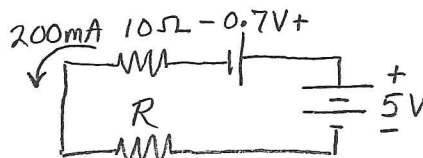
- G) The parameters of the diode in the circuit below are $V_f = 0.7$ V and $r_f = 10 \Omega$. The current through the diode is 200 mA. Which of the following is closest to the value of R ?

- a: 1 Ω
 b: 5 Ω
 (c): 10 Ω
 d: 15 Ω
 e: 20 Ω




$$5V - 0.7V - 0.2A(10\Omega + R) = 0$$
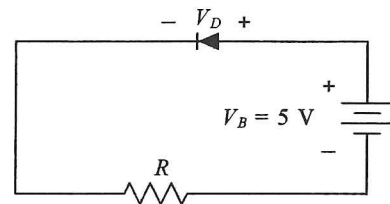
$$R + 10\Omega = \frac{4.3V}{0.2A} = 21.5\Omega \Rightarrow R = 21.5\Omega - 10\Omega = 11.5\Omega$$



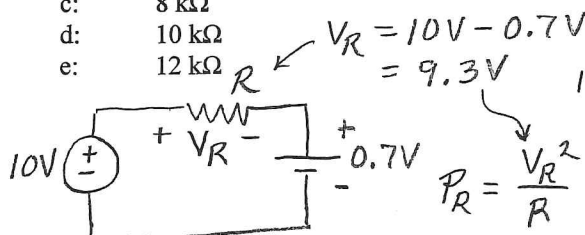- H) The parameters of the diode in the circuit below are $V_f = 0.7$ V and $r_f = 0$. If $V_{PS} = 10$ V and the resistor dissipates 14 mW, which of the following is closest to the value of R ?

- a: 4 k Ω
 (b): 6 k Ω
 c: 8 k Ω
 d: 10 k Ω
 e: 12 k Ω




Note $10V \geq 0.7V \Rightarrow$ Forward-bias

$$V_R = 10V - 0.7V = 9.3V$$


$$P_R = \frac{V_R^2}{R} \Rightarrow R = \frac{V_R^2}{P_R}$$
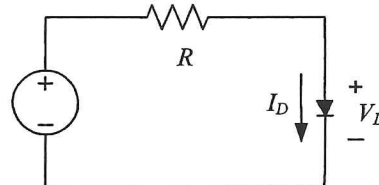
$$\Rightarrow R = \frac{(9.3V)^2}{14mW} \cong 6.18k\Omega$$



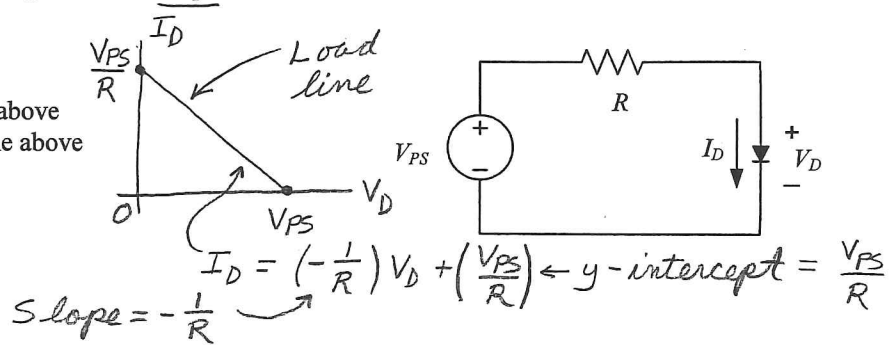
- I) The parameters of the diode in the circuit below are $V_f = 0.6 \text{ V}$ and $r_f = 10 \Omega$, and $V_{PS} = 10.0 \text{ V}$. Which of the following affects the slope of the load line for this circuit?

- a: V_f
b: r_f
c: V_{PS}
d: All of the above
e: None of the above




- J) The parameters of the diode in the circuit below are $V_f = 0.7 \text{ V}$ and $r_f = 0$. Which of the following is closest to the value of I_D ?

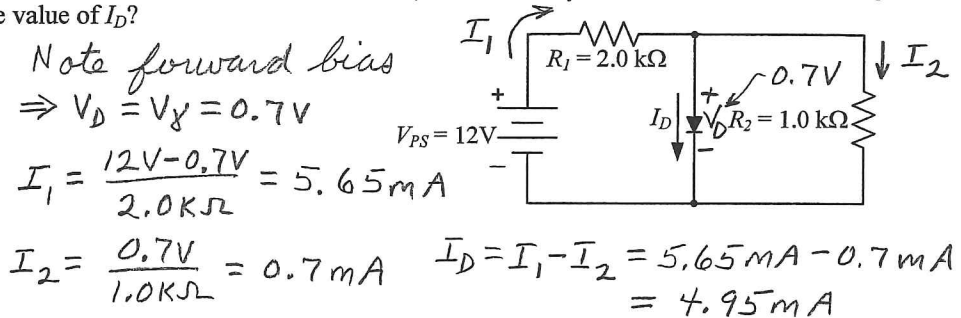- a: 9 mA
b: 8 mA
c: 7 mA
d: 6 mA
e: 5 mA





- K) The parameters of the diode in the circuit below are $V_f = 0.7 \text{ V}$ and $r_f = 5 \Omega$. If the battery voltage is increased to 12 V , which of the following changes will occur to the amplitudes of the AC and DC components of the diode's voltage, $v_D(t)$?

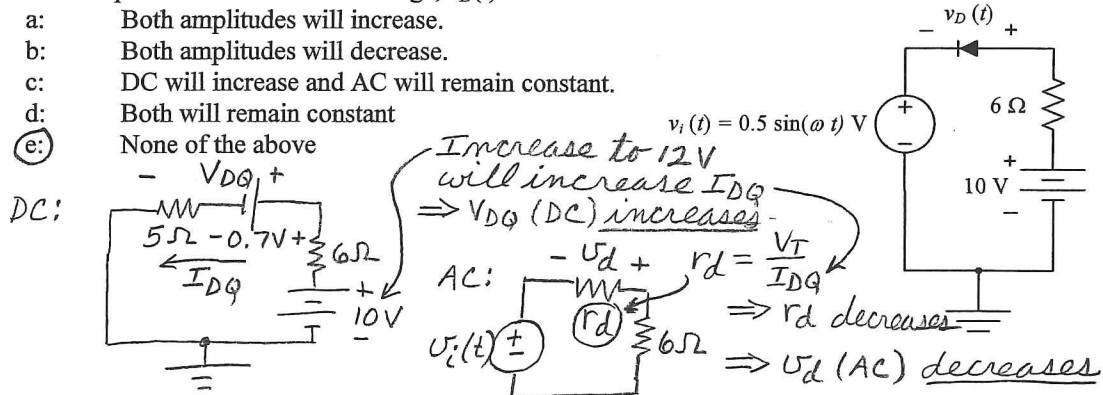- a: Both amplitudes will increase.
b: Both amplitudes will decrease.
c: DC will increase and AC will remain constant.
d: Both will remain constant
e: None of the above



- L) The parameters of the diode in the circuit below are $V_f = 0.7 \text{ V}$ and $r_f = 0$. Which of the following components should be used to model the diode in the circuit's small-signal, ac representation?

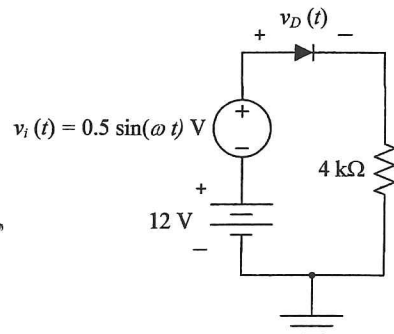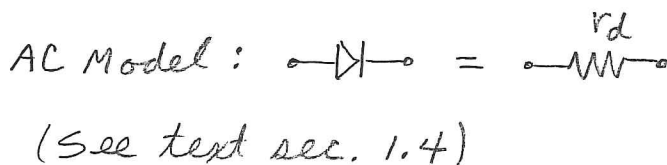- a: A dc voltage source
b: A dc voltage source in series with a resistor
c: A resistor
d: An ac voltage source in series with a resistor
e: None of the above



- M) Which of the following is the principal reason why current flows when a reverse-biased photodiode is exposed to light?
- a: Light creates excess free electrons in the n-region.
 - b:** Light creates excess free electrons and holes in the space-charge region.
 - c: Light creates excess holes in the p-region.
 - d: All of the above
 - e: None of the above


see text sec. 1.5

- N) Which of the following devices are usually fabricated from direct bandgap materials?
- a: Zener diodes
 - b: Schottky barrier diodes
 - c:** light-emitting diodes
 - d: photodiodes
 - e: None of the above


see text sec. 1.5.3

(Electron-hole recombination usually does not produce photons (light) unless the diode is made from direct bandgap material.)

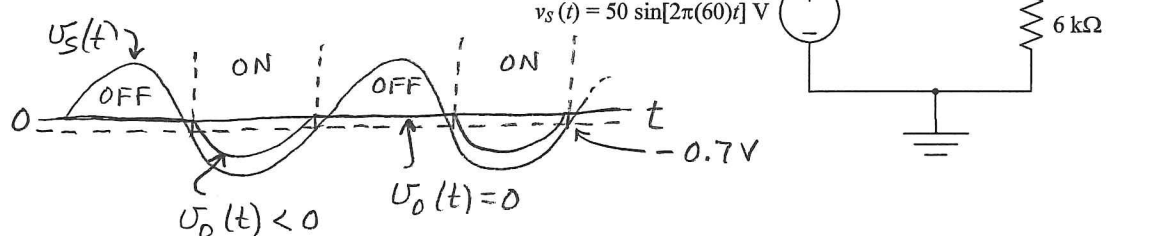- O) The parameters of the diode in the circuit below are $V_f = 0.7$ V and $r_f = 0$. Which of the following is true for $v_o(t)$?
- a: $v_o(t)$ is always negative.
 - b:** $v_o(t)$ is sometimes negative and sometimes zero.
 - c: $v_o(t)$ is always positive.
 - d: $v_o(t)$ is sometimes positive and sometimes zero.
 - e: None of the above



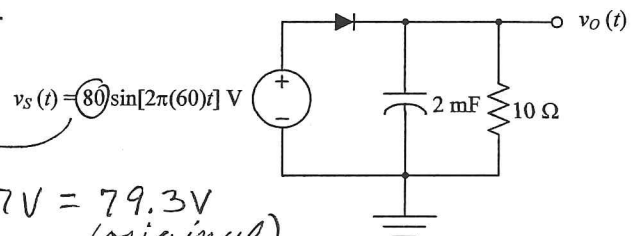- P) The cut-in voltage of the diode in the circuit shown below is 0.7 V. Which of the following will occur if the amplitude of $v_s(t)$ is reduced to 40 V?
- a: The maximum value of $v_o(t)$ will decrease.
 - b: The ripple voltage will decrease.
 - c:** Both a and b will occur.
 - d: The diode's peak current will increase.
 - e: None of the above



Max value of $v_o(t) = 80\text{ V} - 0.7\text{ V} = 79.3\text{ V}$ (original)


New max value = $40\text{ V} - 0.7\text{ V} = 39.3\text{ V} = V_m$ (decreases)

Ripple voltage $V_r = \frac{V_m}{fRC} \Rightarrow V_r$ also decreases

- Q) The parameters of the diodes in the circuit below are $V_f = 0.7 \text{ V}$ and $r_f = 0$. The voltage source v_s is a sine wave whose amplitude is 5 V . Which of the following is closest to the peak inverse voltage for diode D_1 ?

- a: 11 V
 b: 9 V *PIV for D_1 occurs*
 c: 7 V *when $v_s = -5 \text{ V}$*
 d: 5 V
 e: 3 V $\Rightarrow D_1$ off and D_2 on
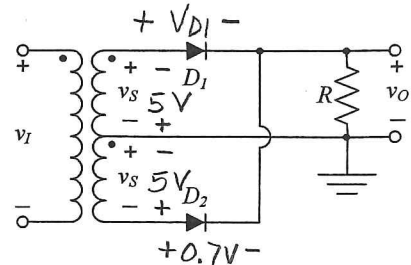
$$\begin{aligned} \text{KVL: } V_{D1} &= -5 \text{ V} - 5 \text{ V} - (-0.7 \text{ V}) \\ \Rightarrow V_{D1} &= -10 \text{ V} + 0.7 \text{ V} = -9.3 \text{ V} \\ \Rightarrow \text{PIV} &= 9.3 \text{ V} \end{aligned}$$




- R) In the circuit shown below, $R_i = 50 \Omega$, $V_Z = 7 \text{ V}$, and $V_{PS} = 12 \text{ V}$. If a resistor R_L is placed in parallel with the diode, which of the following is closest to the value of R_L that will cause I_Z to drop to half of its original value?

- a: 50Ω
 b: 80Ω *original $I_Z = I_I$*
 c: 110Ω
 d: 140Ω $= \frac{12 \text{ V} - 7 \text{ V}}{50 \Omega} = 0.1 \text{ A}$
 e: 170Ω

$$\text{New } I_Z = \frac{1}{2}(0.1 \text{ A}) = 0.05 \text{ A}$$

$$\Rightarrow I_L = I_I - I_Z = 0.1 \text{ A} - 0.05 \text{ A} = 0.05 \text{ A}$$
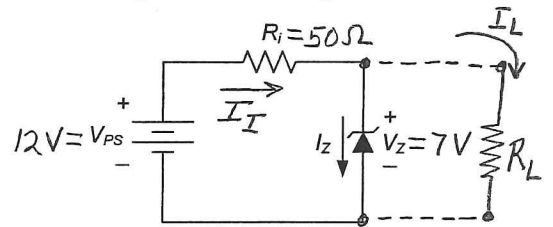
$$\Rightarrow R_L = \frac{7 \text{ V}}{0.05 \text{ A}} = 140 \Omega$$



- S) In the circuit shown below, $R_i = 50 \Omega$, $V_Z = 6 \text{ V}$, and R_L varies between 60Ω and 80Ω . The power dissipated by the diode must not exceed 290 mW . Which of the following is closest to the maximum permissible value of V_{PS} ?


- a: 8 V $P_Z(\text{max}) = 290 \text{ mW} = V_Z I_Z(\text{max})$
 b: 9 V
 c: 10 V $\Rightarrow I_Z(\text{max}) = \frac{290 \text{ mW}}{6 \text{ V}} \cong 48.3 \text{ mA}$
 d: 11 V
 e: 12 V $I_Z = I_Z(\text{max})$ when $V_{PS} = V_{PS}(\text{max})$

$$\text{and } R_L = R_L(\text{max}) = 80 \Omega$$

$$\text{When } R_L = 80 \Omega, I_L = \frac{6 \text{ V}}{80 \Omega} = 0.075 \text{ A} = 75.0 \text{ mA}$$

$$\text{and } I_I = I_Z + I_L \cong 48.3 \text{ mA} + 75.0 \text{ mA} = 123.3 \text{ mA}$$

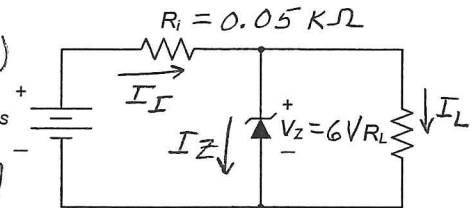
$$\Rightarrow V_{PS}(\text{max}) \cong (123.3 \text{ mA})(0.05 \text{ k}\Omega) + 6 \text{ V} \cong 12.17 \text{ V}$$



- T) In the circuit shown below, V_{PS} varies between 18 V and 20 V , $V_Z = 12 \text{ V}$, and R_L varies between 50Ω and 70Ω . Which of the following conditions will minimize the diode's current?

- a: $V_{PS} = 20 \text{ V}$ and $R_L = 50 \Omega$
 b: $V_{PS} = 20 \text{ V}$ and $R_L = 70 \Omega$
 c: $V_{PS} = 18 \text{ V}$ and $R_L = 50 \Omega$
 d: $V_{PS} = 18 \text{ V}$ and $R_L = 70 \Omega$
 e: None of the above

See text sec. 2.2.1

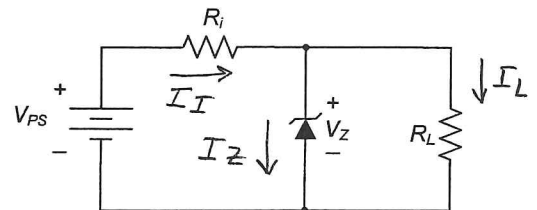

$$I_Z = I_Z(\text{min}) \text{ when } V_{PS} = V_{PS}(\text{min}) \text{ and } I_L = I_L(\text{max}) \Rightarrow R_L = R_L(\text{min})$$