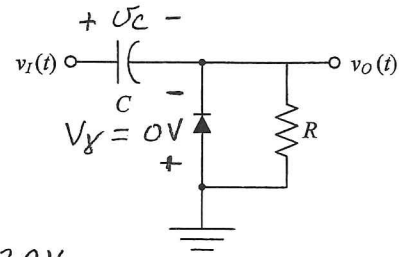


ECE 3200
Test 2
Solutions

- A) The parameters of the diode in the circuit below are $V_f = 0$ and $r_f = 0$. The input voltage $v_I(t) = 20 \sin[2\pi(60)t]$ V, and the capacitor is uncharged at $t = 0$. Which of the following is closest to the maximum value of $v_O(t)$ after the capacitor becomes fully charged?


- a: 40 V
 b: 30 V
 c: 20 V
 d: 10 V
 e: 0 V
- (Clamper circuit)*
Capacitor charges fully when $v_I(t) = -20V$
 $\Rightarrow V_C = -20V (\text{max})$

$$\Rightarrow v_O(t) (\text{max}) = v_I(t) (\text{max}) + 20V = 20V + 20V = 40V$$



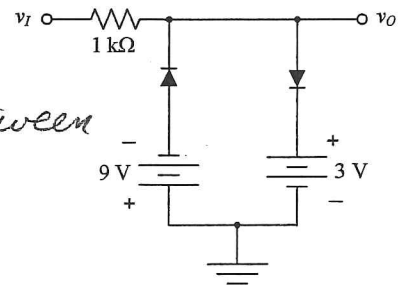- B) The parameters of the diodes in the circuit below are $V_f = 0.7$ V and $r_f = 0$. Which of the following are possible values of the output voltage v_O ?

- a: 8 V
 b: 6 V
 c: Both a and b
 d: -10 V
 e: None of the above
- (Parallel-based clipper)*
 v_O must stay between $-9V - V_f = -9.7V$ and $3V + V_f = 3.7V$



- C) Which of the following is used to shift the dc level of a signal voltage without modifying the shape of the signal's waveform?

- a: Clipper
 b: Rectifier
 c: Clamper
 d: Passive limiter
 e: Voltage doubler

See text sec. 2.3.2


- D) The parameters of the diodes in the circuit below are $V_f = 0.7$ V and $r_f = 0$. Which of the following is closest to the value of the output voltage v_O when $v_I = 0$ V?

- a: 6.0 V
 b: 4.5 V
 c: 3.0 V
 d: 1.5 V
 e: 0 V
- Assume D2 is off.*
 $10V - v_I = 10V \geq V_f \Rightarrow D1 \text{ is on.}$
 $\Rightarrow V_{D1} = V_f = 0.7V$

$$\Rightarrow v_O = \left(9.3V \frac{1k\Omega}{11k\Omega} \right) + 0.7V \approx 1.55V$$


$$\Rightarrow V_{D2} \approx 5V - 1.55V = 3.45V > V_f = 0.7V$$
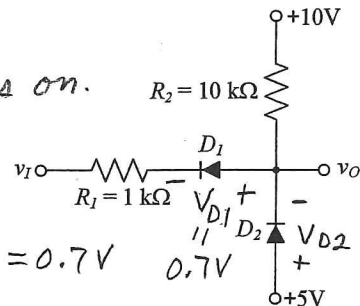
$$\Rightarrow D2 \text{ is ON} \Rightarrow V_{D2} = 0.7V \Rightarrow v_O = 5V - 0.7V = 4.3V$$



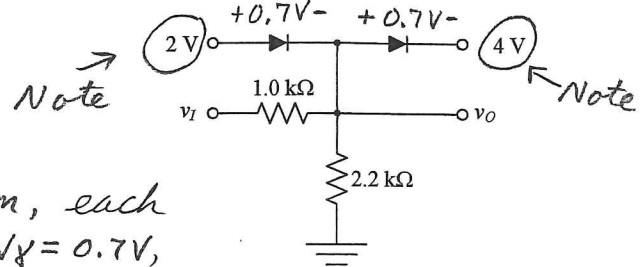- E) The parameters of the diodes in the circuit below are $V_f = 0.7\text{ V}$ and $r_f = 0$. Which of the following conditions is impossible for this circuit?

- a: Both diodes are off.
 b: Both diodes are on.
 c: One diode is on and the other is off.
 d: The output voltage is positive.
 e: Current flows through both resistors.



If both diodes were on, each would have a drop of $V_f = 0.7\text{ V}$, but $2\text{ V} - 4\text{ V} \neq 2(0.7\text{ V}) = 1.4\text{ V}$

- F) The base-collector junction of a bipolar transistor is reverse biased. Which of the following must be true?

- a: The transistor is in the forward-active mode.
 b: The transistor is in either the forward-active mode or cutoff.
 c: The transistor is in the saturation mode.
 d: The transistor is in either the forward-active mode or saturation.
 e: None of the above

*Forward - active mode: B-E is forward biased, B-C is reverse biased
 cutoff: Both junctions reverse biased*

- G) A bipolar junction transistor has an Early voltage of 80 V. Its collector current is 0.60 mA when $V_{CE} = 2\text{ V}$ for a certain base current. If its base current remains constant, which of the following is closest to the value of the transistor's collector current when $V_{CE} = 5\text{ V}$?

- a: 0.618 mA
 b: 0.622 mA
 c: 0.626 mA
 d: 0.630 mA
 e: 0.634 mA

$$r_o = \frac{V_A}{I_{CQ}} = \frac{80\text{ V}}{0.60\text{ mA}} \approx 133.3\text{ k}\Omega$$

$$\Delta I_C = \frac{\Delta V_{CE}}{r_o} \approx \frac{(5\text{ V} - 2\text{ V})}{133.3\text{ k}\Omega} \approx 0.0225\text{ mA}$$

$$\Rightarrow I_C(\text{new}) \approx 0.60\text{ mA} + 0.0225\text{ mA} = 0.6225\text{ mA}$$

- H) The common-base current gain of a bipolar junction transistor is equal to 0.993. If the base current is 10 μA and the transistor is in saturation, which of the following is a possible value of the collector current?

- a: 1.0 mA
 b: 1.5 mA
 c: 2.0 mA
 d: Both b and c
 e: None of the above

$$\alpha = 0.993$$

$$\beta = \frac{\alpha}{1 - \alpha} = \frac{0.993}{1 - 0.993} \approx 141.86$$

$$\text{In saturation, } I_C < \beta I_B$$

$$\Rightarrow I_C < (141.86)(0.010\text{ mA}) \approx 1.42\text{ mA}$$

- I) An npn transistor having $\beta = 120$ has an open-emitter breakdown voltage BV_{CBO} of 200 V. If the empirical constant is $n = 3$, which of the following is closest to the open-base breakdown voltage BV_{CEO} ?

- a: 50 V
 (b): 40 V
 c: 30 V
 d: 20 V
 e: 10 V

$$BV_{CEO} = \frac{BV_{CBO}}{\sqrt[n]{\beta}}$$

$$= \frac{200V}{\sqrt[3]{120}} \approx 40.5V$$

- J) In the circuit shown below, all resistors have values of 1 k Ω , and $\beta = 90$ for the transistor. Which of the following is closest to the value of the collector current?

- a: 25 mA
 b: 20 mA
 c: 15 mA
 d: 10 mA
 (e): 5 mA


Maximum possible I_C flows in saturation (when $V_{CE} = V_{CE(sat)}$)

$$\Rightarrow I_C(max) = \frac{5V - 0.2V}{1K\Omega} = 4.8mA$$

(It is impossible for I_C to be larger)



$$\text{Check: } I_B = \frac{5V - 0.7V}{1K\Omega} = 4.3mA$$
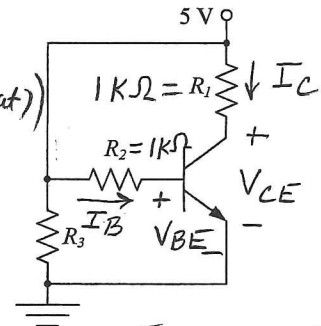
$$\beta I_B = (90)(4.3mA) = 387mA \Rightarrow I_C < \beta I_B \checkmark \text{ (Saturation)}$$



- K) The collector current for the transistor in the circuit below is 5 mA. Which of the following describes the transistor's operating point?

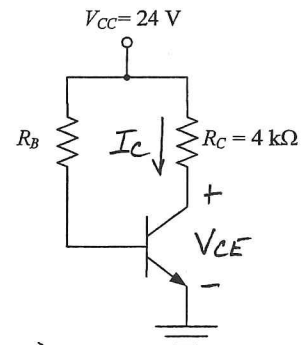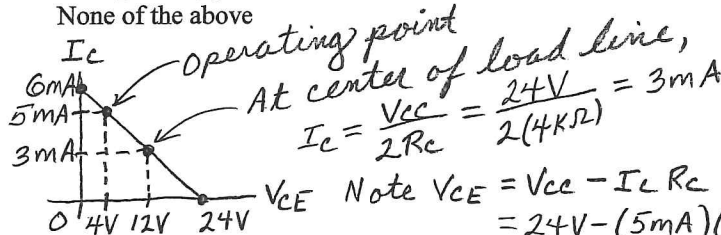- a: The operating point is in the saturation region.
 (b): The operating point is above the center of the load line.
 c: The operating point is at the center of the load line.
 d: The operating point is below the center of the load line.
 e: None of the above



- L) In the circuit shown below, $R_1 = 300$ k Ω , $R_2 = 2$ k Ω , and $\beta = 100$ for the transistor. Which of the following is closest to the value of the collector voltage (V_C)?

- a: 8 V
 (b): 6 V
 c: 4 V
 d: 2 V
 e: 0 V

Assume forward-active mode

$$\Rightarrow V_{EB} = V_{EB(on)} = 0.7V$$


$$\Rightarrow I_B = \frac{9V - 0.7V}{300K\Omega} \approx 0.0277mA$$

$$I_C = \beta I_B \approx (100)(0.0277mA) = 2.77mA$$

$$V_C = I_C R_2 \approx (2.77mA)(2K\Omega) = 5.53V$$

$$\text{Check: } V_{EC} \approx 9V - 5.53V = 3.47V > 0.2V \checkmark$$


(Not in saturation)

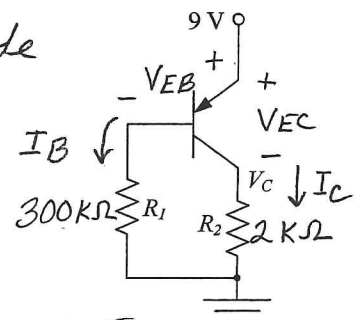

- M) An npn bipolar junction transistor is to be used as a switch to control current flowing through an electric motor. The transistor will be connected between terminals 1 and 2 in the diagram below. Which transistor terminals will be connected to terminals 1 and 2 in the circuit?

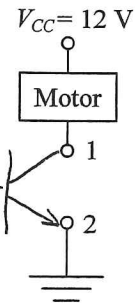
- (a) 1 connects to collector and 2 connects to emitter
 b: 1 connects to collector and 2 connects to base
 c: 1 connects to base and 2 connects to emitter
 d: 1 connects to base and 2 connects to collector
 e: None of the above

(npn transistor as switch) →
 See text sec. 5.3.1





- N) For the transistor in the circuit shown below, $\beta = 90$. The transistor is intended to function as a switch, but the circuit has been designed incorrectly. Which of the following changes would correct the design?

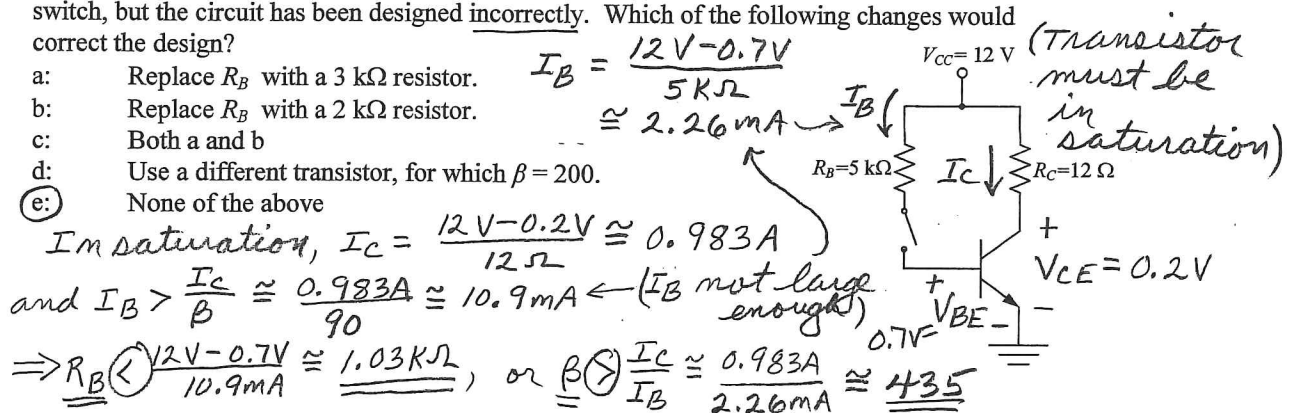- a: Replace R_B with a 3 k Ω resistor.
 b: Replace R_B with a 2 k Ω resistor.
 c: Both a and b
 d: Use a different transistor, for which $\beta = 200$.
 (e) None of the above



- O) The values of the resistors in the circuit below have been chosen to set the transistor's operating point at the center of the load line. If the value of β decreases, which of the following will occur?

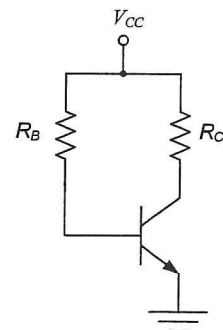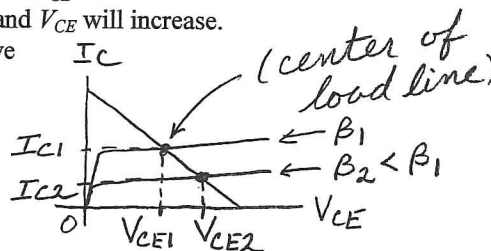- a: Both I_C and V_{CE} will increase.
 b: Both I_C and V_{CE} will decrease.
 c: I_C will increase and V_{CE} will decrease.
 (d) I_C will decrease and V_{CE} will increase.
 e: None of the above




- P) The circuit below is an audio amplifier. Which of the following should be true for capacitor C_C ?

- a: Its impedance should be low at DC.
 b: Its impedance should be high at audio frequencies.
 c: both a and b
 (d) Its impedance should be low at audio frequencies.
 e: None of the above

(See text sec. 5.4.1)

$$\text{Impedance} = \frac{1}{j\omega C_C} = \infty @ \text{DC } (\omega = 0)$$

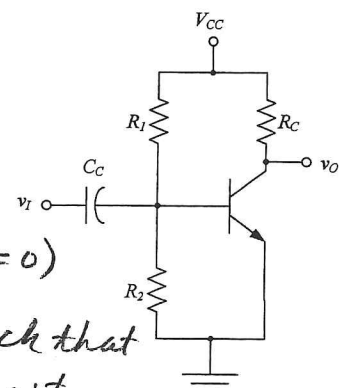C_C should be sufficiently large such that $\frac{1}{\omega C_C}$ is small for signals of interest (i.e. audio frequencies, ω).



- Q) A pnp BJT is biased in the forward-active mode. If $\beta > 100$, and the diffusion resistance of the emitter-base junction is less than $4 \text{ k}\Omega$, which of the following is true?

- a: $g_m > 25 \text{ mA/V}$
 b: $g_m < 25 \text{ mA/V}$
 c: $g_m > 40 \text{ mA/V}$
 d: $g_m < 40 \text{ mA/V}$
 e: None of the above

$$g_m = \frac{\beta}{r_\pi} \leftarrow \begin{matrix} > 100 \\ < 4 \text{ k}\Omega \end{matrix}$$

$$\Rightarrow g_m > \frac{100}{4 \text{ k}\Omega} = 25 \frac{\text{mA}}{\text{V}}$$

- R) A voltage amplifier whose output resistance is R_o drives a load whose resistance is R_L . Which of the following conditions normally would be desired in this situation?


- a: R_o is large and R_L is small.
 b: R_o is small and R_L is large.
 c: R_o and R_L are both large.
 d: R_o and R_L are both small.
 e: None of the above

See text sec. 6.3

$R_o \ll R_L$ is preferred for a voltage amplifier.

- S) For the transistor in the circuit below, $V_A = 100 \text{ V}$ and $\beta = 150$. The transistor's temperature is 300 K , its quiescent base current is $10.0 \mu\text{A}$, and the capacitors have negligible impedance at signal frequencies. Which of the following is closest to the small-signal ac voltage gain of the circuit?

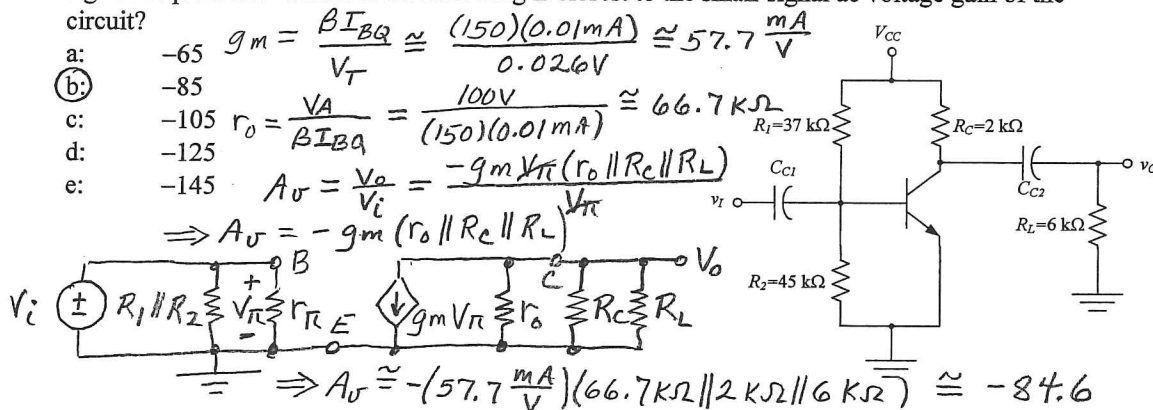- a: -65 $g_m = \frac{\beta I_{BQ}}{V_T} \approx \frac{(150)(0.01 \text{ mA})}{0.026 \text{ V}} \approx 57.7 \frac{\text{mA}}{\text{V}}$
 b: -85
 c: -105 $r_o = \frac{V_A}{\beta I_{BQ}} = \frac{100 \text{ V}}{(150)(0.01 \text{ mA})} \approx 66.7 \text{ k}\Omega$
 d: -125
 e: -145 $A_v = \frac{v_o}{v_i} = \frac{-g_m V_{\pi} (r_o \parallel R_c \parallel R_L)}{V_{\pi}}$



- T) If the circuit below is modified by adding an emitter resistor, which of the following will happen?

- a: Both R_i and $|A_v|$ will increase.
 b: Both R_i and $|A_v|$ will decrease.
 c: R_i will decrease and $|A_v|$ will increase.
 d: R_i will increase and $|A_v|$ will decrease.
 e: None of the above

See text sec. 6.4.2

