

## BJT Common-Emitter Design II

Christopher Brant, ECE 3110(4), November 27<sup>th</sup>, 2017

### Equations

$$R_{ac} = (R_C \parallel R_L)$$

Equation 1: Rac resistance

$$|I_{CQ}| = \frac{nV_T |A_v|}{(R_C \parallel R_L)} = \frac{2nV_T |A_v|}{R_C} = \frac{2nV_T |A_v|}{R_L} = \frac{0.06V |A_v|}{R_L}$$

$$V_{CEQ} = I_{CQ} R_{ac} = \frac{I_{CQ} R_C}{2} = \frac{I_{CQ} R_L}{2}$$

Equations 2 and 3: Q-point values

$$h_{ie} = \frac{V_T}{I_{BQ}} = \beta \frac{V_T}{I_{CQ}} = \beta h_{ib} = r_\pi$$

Equations 4 and 5: hie and hib

$$R_{dc} = \frac{V_{CC} - V_T |A_v|}{I_{CQ}}$$

Equation 6: Rdc resistance

$$R_E = R_{dc} - R_C = R_{dc} - R_L$$

Equation 7: Emitter Resistor value

$$R_B = 0.1 \beta R_E$$

Equation 8: Base Resistor value

$$V_{BB} = V_{BE} + I_{BQ} R_B + I_{CQ} R_E$$

Equation 9: Base Voltage Calculation

$$R_1 = R_B \cdot \frac{V_{CC}}{V_{BE}}$$

$$R_2 = \frac{R_B}{\left(1 - \frac{V_{BE}}{V_{CC}}\right)}$$

Equations 10 and 11: Voltage Divider Biasing Resistor Values

### Simulations for Expected Results

\*Using the values below, all simulations were done as the lab manual has stated\*

- $\beta = 205$ ,  $V_{BE} = 0.68 \text{ V}$ ,  $A_V = -100$
- $R_C = R_L = 4.7 \text{ k}\Omega$ ,  $V_{CC} = 10 \text{ V}$
- $R_{ac} = 2350 \Omega$  and  $R_{dc} = 5795 \Omega$
- $I_{CQ} = 1.277 \text{ mA}$  and  $V_{CEQ} = 3 \text{ V}$
- $h_{ie} = r_\pi = 4173.84 \Omega$  and  $h_{ib} = 20.36 \Omega$
- $R_E = 1095 \Omega$
- $R_B = 22444 \Omega$
- $V_{BB} = 2.218 \text{ V}$
- $R_1 = 101185 \Omega$
- $R_2 = 28840 \Omega$
- Assuming a  $V_{i-pp}$  of  $\sim 0.02 \text{ V}$ , with a voltage gain of  $-100$ , the  $V_{o-pp}$  should be  $\sim 2 \text{ V}$
- Although the above mentioned values are all mathematically correct and derived, assuming  $R_C$  is  $4.7 \text{ k}\Omega$  and  $R_L$  is also  $4.7 \text{ k}\Omega$ , the corresponding simulations that are shown below do not reflect what is expected from a voltage gain of  $-100$ .

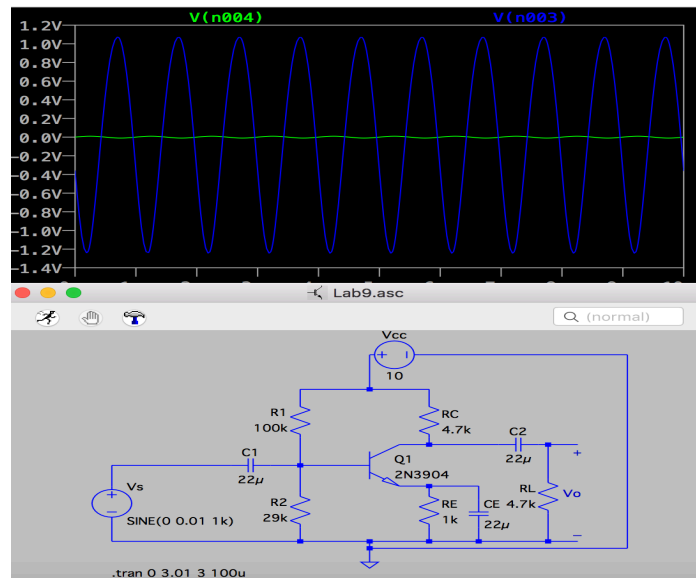


Figure 1: Simulation for Figure 9.1 with the above calculated values ( $V_s$  in green and  $V_o$  in blue)